

# NYCU-EE IC LAB - Spring 2023

## Lab06 Practice

### Design: Complex Multiplier (Genvar Version)

#### Objective

This practice will guide you to use different **genvar** statement in different kind of scenario.


#### Data Preparation

1. Extract test data from TA's directory:  
`% tar xvf ~iclabta01/Lab06.tar`
2. The extracted LAB directory contains:
  - a. **00\_TESTBED**
  - b. **01\_RTL**
  - c. **02\_SYN**
  - d. **03\_GATE**

#### Design Description

Design a complex number multiplier with genvar method as practice.

Circuit Architecture: **GENVAR\_PRAC.v**

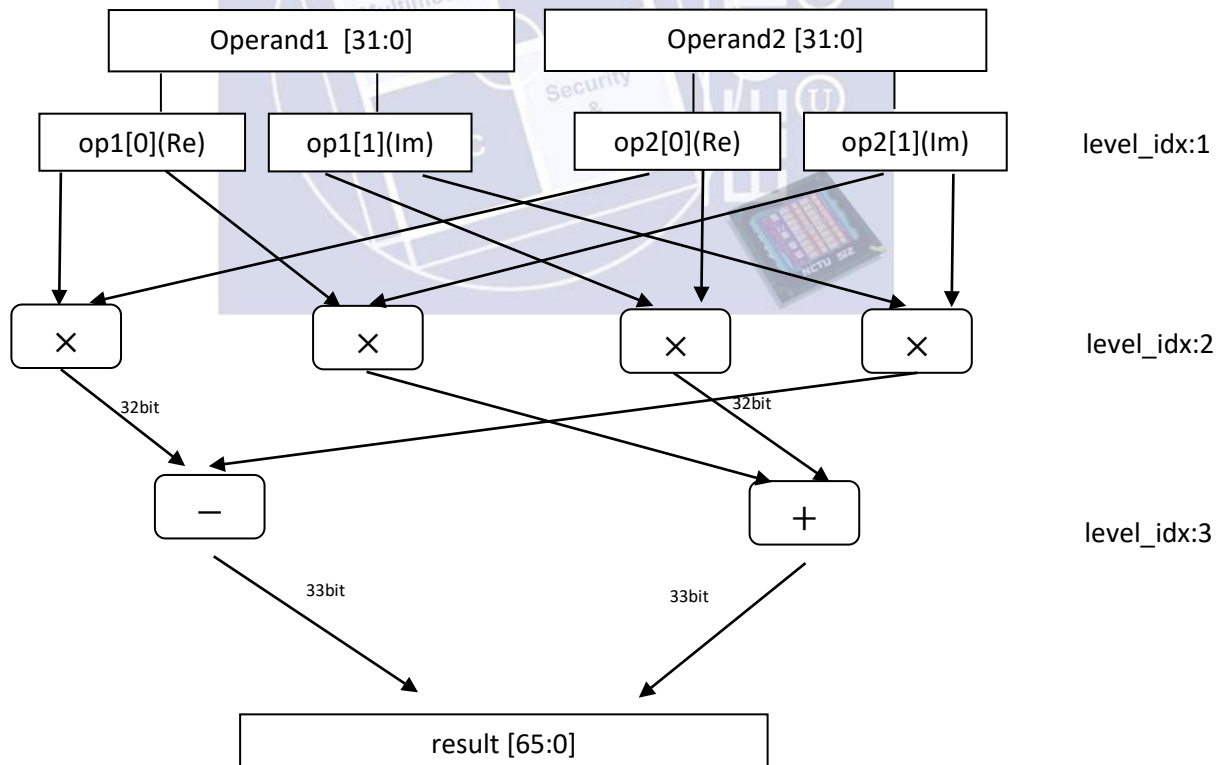

## Inputs and Outputs

Input signal	Bit width	Definition
operand1	32	Input operand1 {real[15:0],imagine[15:0]}
operand2	32	Input operand2 {real[15:0],imagine[15:0]}


Output signal	Bit width	Definition
result	66	Output number {real[32:0],imagine[32:0]}

**COMPLEX\_MULT.v** : Just wrapper to demonstrate for using your own IP

**GENVAR\_PRAC.v** : To practice genvar statement
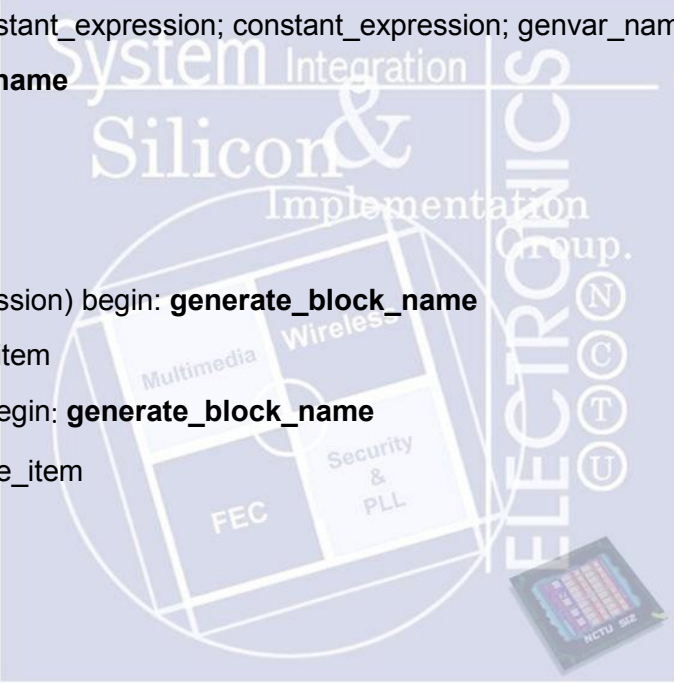
## Syntax

```
for (genvar_name = constant_expression; constant_expression; genvar_name = constant_expression)
begin: generate_block_name
    generate_item
    generate_item
    ...
    if (constant_expression) begin: generate_block_name
        generate_item
        for (.....) begin: generate_block_name
            generate_item
        end
    end
end
end
```



## Summary

1. wire or reg: could be instantiated in the **for loop** or **if loop**
2. if-else condition could only apply for genvar variable
3. each iteration has only the scope of that iteration. To access previous iteration's item , you must specify the item hierarchically by using generate\_block\_name.
4. Strongly Recommend using nWave to see the architecture of your genvar statement design.

## Version