

# NCTU-EE IC LAB – Fall 2022

## Lab02 Practice

### Design: Complex Number Calculator

#### Data Preparation

---

1. Extract test data from TA's directory:  
`% tar xvf ~iclabta01/Lab02.tar`
2. The extracted LAB director contains:
  - a. Exercise
  - b. Practice

#### Design Description

---

Complex numbers are widely used in engineering field, such as communications, circuit designs, or waveform analysis. A complex number contains a real part  $a$  and an imaginary part  $b$ , which can be denoted in  $a+bi$ . Now you are going to implement a complex number calculator, which can perform addition, subtraction and multiplication to two complex numbers  $a+bi$  and  $c+di$ . The arithmetic result  $e+fi$  will be: addition:  $(a+c) + (b+d)i$ , subtraction:  $(a-c) + (b-d)i$ , and multiplication:  $(ac-bd) + (ad+bc)i$ . Try to implement the calculator as small as possible.

#### Inputs

---

1. You will receive a sequence of 8-bit 2's complement *signed numbers*  $IN[7:0]$  with length 4, representing  $a$ ,  $b$ ,  $c$  and  $d$  in order sequentially. The input values' range is -128~127.
2. The sequence with length 4 is valid when  $IN\_VALID$  is high.
3.  $MODE$  is valid when the *first cycle* of  $IN\_VALID$  is high.  
MODE 0: **Addition**  
MODE 1: **Subtraction**  
MODE 2: **Multiplication**
4. There is *only 1 reset* before the first pattern, thus, your design must be able to reset automatically.
5. All inputs will be changed at clock *negative* edge.
6. The next input pattern will come in 1~3 cycles after  $OUT\_VALID$  falls.

## Outputs

1. You have to output a sequence of 17-bit **2's complement signed numbers** **OUT[16:0]** in consecutive 2 cycles, representing **e** and **f** respectively.
2. All outputs are synchronized at clock **positive** edge.
3. **OUT\_VALID** should be low after initial reset.
4. **OUT\_VALID** should not be raised when **IN\_VALID** is high.
5. **OUT\_VALID** is set to high when the output value is valid.
6. The test pattern will check whether your output sequence is correct or not at clock **negative** edge.

## Specifications

1. Top module name : **CNC** (File name : **CNC.v**)
2. Input pins: **clk**, **rst\_n**, **IN\_VALID**, **IN[7:0]**, **MODE**
3. Output pins: **OUT\_VALID**, **OUT[16:0]**
4. It is **synchronous** reset and **active-low** architecture.
5. All numbers are represented in **2's complement signed number** format, so you have to do sign extension whenever necessary.
6. The latency of your design in each pattern should not be larger than **100** cycles. The latency is defined in Fig.1.<sup>a</sup>
7. The clock period is set to **6ns**, and both input and output delay are set to **3ns**.
8. The output loading is set to 0.05.
9. The synthesis result of data type cannot include any **LATCH** (in syn.log).
10. After synthesis, you can check **CNC.area**, **CNC.timing** and **CNC.resource**.
11. The slack in the end of **CNC.timing** should be **non-negative** and the result should be **MET**.


Note: If you want to use signed multiplication, both two inputs of the multiplier should be declared with **signed**.

Ex:

```
reg signed [3:0] A;  
reg signed [3:0] B;  
reg [3:0] C;  
reg [7:0] OUT;
```

```
always @* OUT=A*B;           ← signed multiplication  
always @* OUT=A*C;           }  
always @* OUT={A[3], A[3:1]}*B; } ← unsigned multiplication  
always @* OUT=A*{1'b0, A[2:0]}; }
```

## Block Diagram

 

## Note

1. This practice is for practicing the finite state machine (FSM), thus some codes are given; try to complete the codes to achieve the correct result. However, you can implement the design with your own code.

2. Try to use as less hardware as possible.

**Hint: Accumulator can be reused.**

3. Template folders and reference commands:

01\_RTL/ (RTL simulation) **./01\_run**

02\_SYN/ (Synthesis) **./01\_run\_dc**

(Check the design which contains **Latch** or not in **syn.log**)

(Check the design's timing in /Report/CNC.timing)

03\_GATE\_SIM/ (GL simulation) **./01\_run**

You can key in **./09\_clean\_up** to clear all log files and dump files in each folder

4. Sample waveform:

 


Fig.1

$$\begin{aligned}
 &8 \times 5 = 40 \\
 &1000 \times 1000 = 1000000 \\
 &7 \div 1000000
 \end{aligned}$$