

# NYCU-EE IC LAB – Spring 2023

## Lab01 Practice

### Simulation flow

#### Objective

---

We will guide you to simulate RTL design, synthesize design and simulate gate-level design.

#### Reference data

---

1. Use the lecture document that was on the IC Lab course page
2. Ask the TA if you have any questions.

#### Data Preparation


---

1. Extract test data from TA's directory:  
`% tar xvf ~iclabta01/Lab01.tar`

#### Simulation Flow:

---

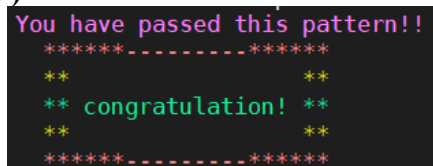1. Enter Lab01/Practice/01\_RTL folder by command  
“cd Lab01/Practice/01\_RTL”
2. Simulate RTL design by command “./01\_run”
3. **Check the simulation result, which represents whether your design functions correctly or not. (You will see congratulation message like this on the terminal if you pass the pattern.)**



```
You have passed this pattern!!
*****-----*****
**                               **
**  congratulation!  **
**                               **
*****-----*****
```

4. Use command “nWave &” to open nWave and check the waveform to debug.  
After finishing RTL design, enter “Lab01/Practice/02\_SYN folder” by command  
“cd ../02\_SYN”
5. Synthesize design by command “./01\_run\_dc”
6. After 02\_SYN simulation done the files of “CORE\_SYN.v”, “CORE\_SYN.sdf”  
would be created under the folder “Lab01/Practice/02\_SYN/Netlist”
7. Enter the “Lab01/Practice/02\_SYN/Report” folder. **Check timing and area report to ensure your design meets the spec.**

Operating Conditions: slow    Library: slow  
Wire Load Model Mode: top

Startpoint: in\_n0[1] (input port)  
Endpoint: out\_n[4] (output port)  
Path Group: default  
Path Type: max

Point	Incr	Path
-----		
input external delay	0.00	0.00 r
in_n0[1] (in)	0.00	0.00 r
U59/Y (NAND2XL)	0.13	0.13 f
U70/Y (INVXL)	0.14	0.27 r
U76/Y (NAND2XL)	0.11	0.38 f
U78/Y (NAND2XL)	0.11	0.49 r
U79/Y (OAI21XL)	0.12	0.61 f
U60/Y (NOR2X1)	0.14	0.74 r
U62/S (ADDFXL)	0.99	1.73 f
U86/Y (NAND2XL)	0.22	1.95 r
U87/Y (MXI2XL)	0.22	2.17 f
U88/Y (AOI2BB2XL)	0.30	2.48 f
U89/Y (AOI21XL)	0.17	2.65 r
U90/Y (INVXL)	0.04	2.69 f
out_n[4] (out)	0.00	2.69 f
data arrival time		2.69
max_delay	30.00	30.00
output external delay	0.00	30.00
data required time		30.00
-----		
data required time		30.00
data arrival time		-2.69
-----		
slack (MET)		27.31

(Be careful!! In the CORE.timing file, slack should be “MET”)

8. Enter 02\_SYN and check the syn.log file to see if there are latches in the design.  
(Be careful!! You can't have latch in your design.)

=====										
Register Name	Type	Width	Bus	MB	AR	AS	SR	SS	ST	
=====										
out_n_reg	Latch	7	Y	N	N	N	-	-	-	
=====										

**Forbidden !!**

9. Enter Lab01/Practice/03\_GATE\_SIM folder  
10. Simulate gate-level design by command “./01\_run”  
11. Check the gate level simulation result, which represents whether your synthesized design functions are correct or not.  
12. Use command “nWave &” to open nWave and check the waveform  
13. Clean the log files and dump files by command “./09\_clean\_up”(Recommended!)

## Design

A simple calculator with addition, subtraction. A module FA is provided, you need to use it to build the two mentioned operations.

INPUT 3 bits: in\_n0, in\_n1.

INPUT 1 bits : opt

OUTPUT 4 bits : out\_n



opt=0 → addition:  $\text{in\_n0} + \text{in\_n1}$




opt=1 → subtraction:  $\text{in\_n0} - \text{in\_n1}$

**You should use the module FA provided in CORE.v to design your calculator.** There's no area constraint for this practice, so feel free to use any number of FAs. However, using the fewest number of FAs to finish the task is recommended.

## Hints

  1. You are not allowed to use arithmetic operation +, -, \* in this practice. Instead, you should use gate-level, for example, the module provided by TA.
2. Example for adding two 3-bits variables:



   

$$\begin{array}{r} \cancel{0}001 \\ \cancel{0}010 \\ \hline 100 \end{array}$$

$$\begin{array}{r} 001 \\ 010 \\ \hline 001 \\ 101 \\ \hline \end{array}$$